

QUESTION BANK

(B.E. SEM III EC ATKT EXAM)

GUJARAT UNIVERSITY

Network Analysis

Each Question of 10 Marks

- Q.1.** Which are the types of energy sources? Explain it.
- Q.2.** Define the following terms:
(1) Linearity (2) Reciprocity (3) Time Invariance (4) Passivity (5) Lumped network (6) Active network (7) Unilateral network (8) Bilateral network (9) Distributed network (10) Time Variance
- Q.3.** Determine current through the 4Ω resistor branch of the given network of figure (1).
- Q.4.** Determine the mesh current I_1 , I_2 , I_3 in the network of figure (2)
- Q.5.** Determine the voltages of nodes 1 and 2 in the network of figure (3)
- Q.6.** Write down source transformation theorem and explain it
- Q.7.** Determine numerical value of I_2 using source transformation method in figure (4).
- Q.8.** Determine current I using source transformation method in figure (5).
- Q.9.** Solve the nodal voltage V_1 , V_2 , V_3 and V_4 as shown in figure (6) using nodal analysis.
- Q.10.** Write down superposition theorem and explain it with an example
- Q.11.** Write down Thevenin's theorem and explain it with an example

- Q.12.** Write down Norton's theorem and explain it with an example
- Q.13.** Write down Reciprocity theorem and explain it with an example
- Q.14.** Derive the expression for maximum power transfer theorem for the following condition: (1) Source and load are resistive (2) Source is complex impedance and load is complex impedance with variable resistance and reactance
- Q.15.** Derive the expression for maximum power transfer theorem for the following condition: (1) Source is complex impedance and load is variable resistance (2) Source is complex impedance and load is variable reactance
- Q.16.** Find the current in 10Ω resistor in the network of figure (7) using thevenin's theorem.
- Q.17.** Write down thevenin's equivalent across load resistance R_L in figure (8).
- Q.18.** Determine the value of I_1 using superposition theorem in figure (9).
- Q.19.** In the network of figure (10) the switch k is closed at $t = 0$ with the capacitor uncharged and with zero current in the Inductor. Find the values of i , di/dt and d^2i/dt^2 at $t=0+$.
- Q.20.** Determine step response to RC series circuit by using Laplace transformation
- Q.21.** Determine step response to RL series circuit by using Laplace transformation
- Q.22.** Define Laplace transformation and explain it to solve differential equations.
- Q.23.** Write down and prove Initial and final value theorem
- Q.24.** Determine the relationship between ABCD and Z parameters
- Q.25.** Determine the relationship between Y and g parameters
- Q.26.** Determine the relationship between h and ABCD parameters
- Q.27.** Determine Laplace transformation of following function
(a) $\sin wt$ (b) $e^{-at} \cos wt$
- Q.28.** Find the Inverse Laplace of the following function

(a) $1 / s (s^2 + 6s + 9)$ (b) $(s - 1) / (S^2 + 3S + 2)$

- Q.29.** What is significance of poles and zeros in Laplace transformation? Explain it.
- Q.30.** Determine voltage response to RC series circuit by using first order differential equation.
- Q.31.** Explain Shifting and Scaling theorem for unit step function.
- Q.32.** Explain Driving point function and write down necessary condition for driving point function.
- Q.33.** Short Note: (a) Bode plot (b) Nyquist's stability criteria
- Q.34.** In the network shown in figure (11), a steady state is reached with switch k open. At $t = 0$, the switch is closed. For the element values given, determine the value of $V_a(0^-)$ and $V_a(0^+)$
- Q.35.** In series RL circuit can be excited by $V(t) = V_m \sin (wt + \theta)$. Find out its complete transient as well as steady state response for current.
- Q.36.** In series RC circuit can be excited by $V(t) = V_m \sin (wt + \theta)$. Find out its complete transient as well as steady state response for current.
- Q.37.** Derive the expression for transformation of derivatives and integrals using Laplace transformation
- Q.38.** Explain Partial fraction expansion and Heaviside's expansion theorem for laplace transform
- Q.39.** Explain phasor diagram for RL, RC and RLC circuits.
- Q.40.** Prove: Y parameter can be add in parallel-parallel connection of two port network

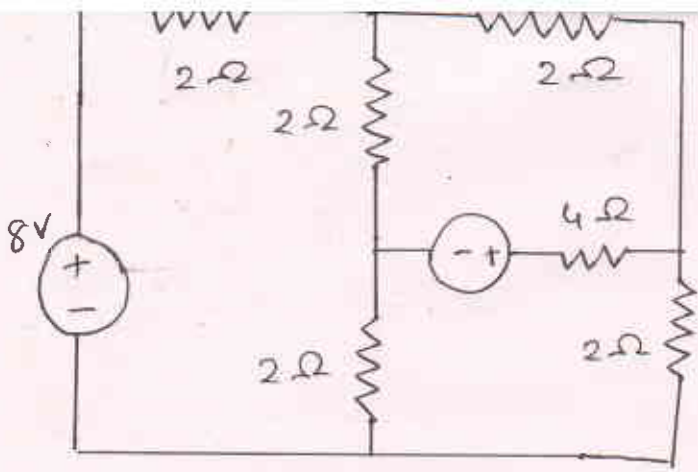


figure (1)

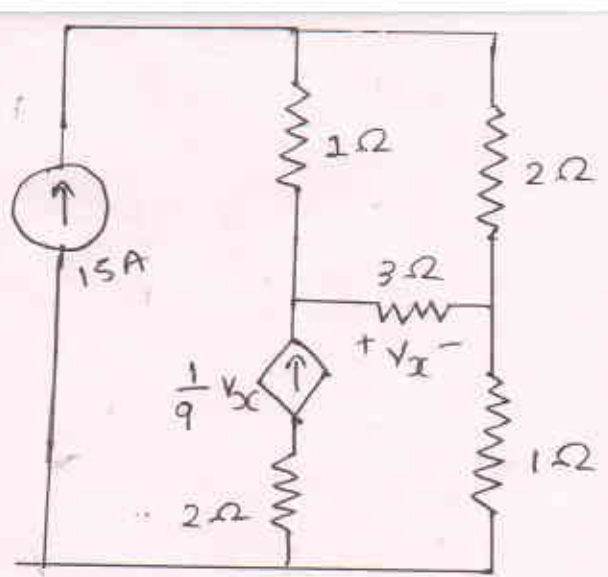


figure (2)

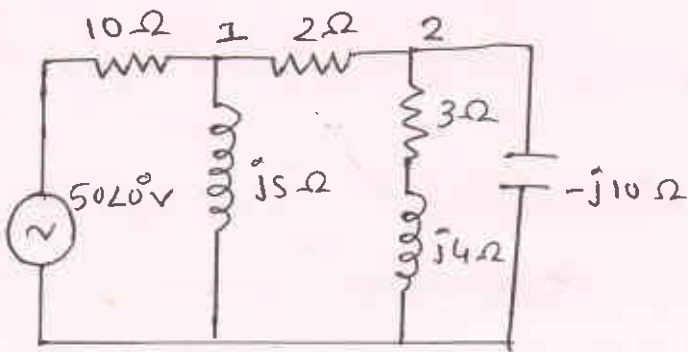


figure (3)

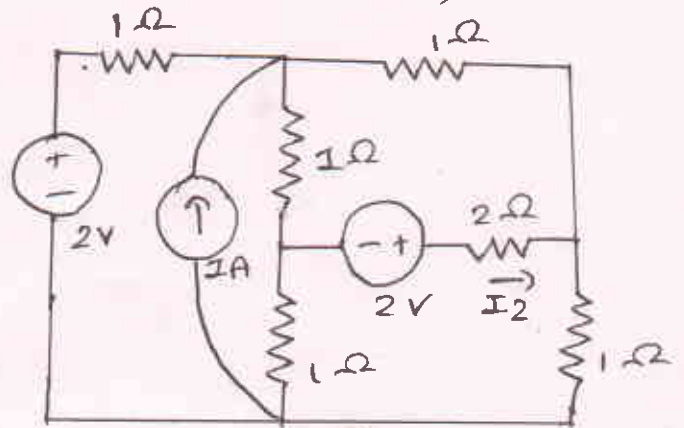


figure (4)

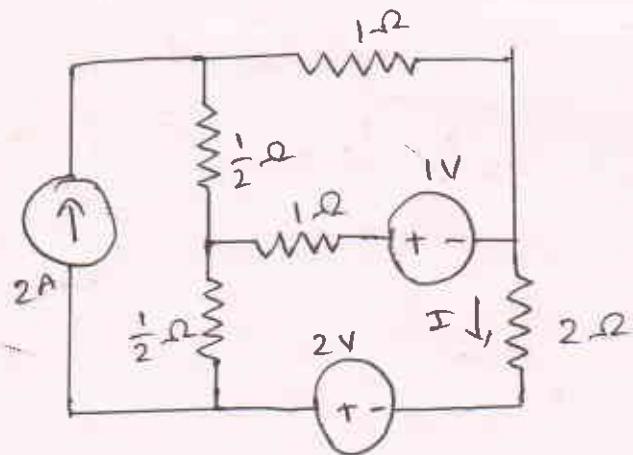


figure (5)

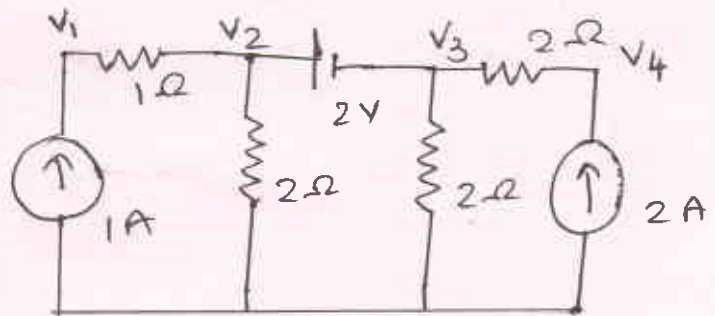


figure (6)

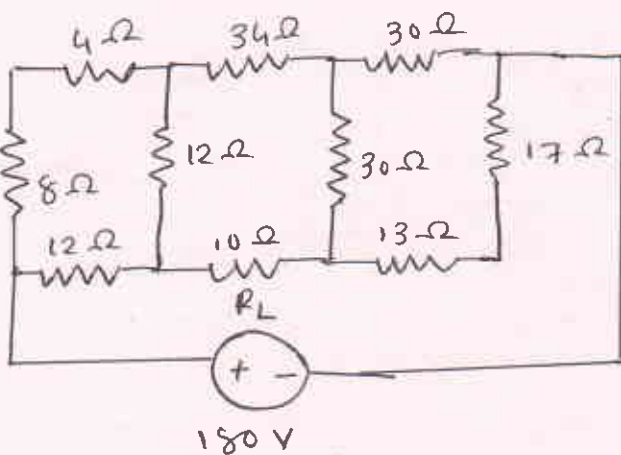


figure (7)

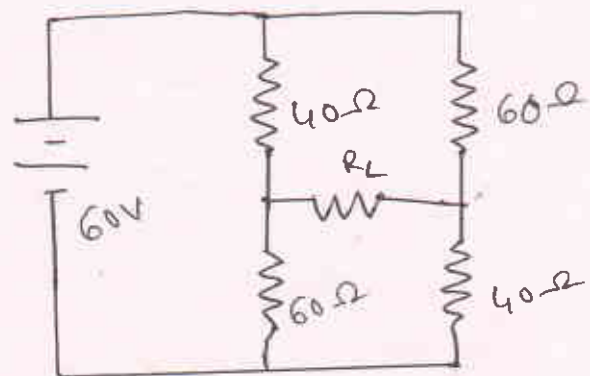


figure (8)

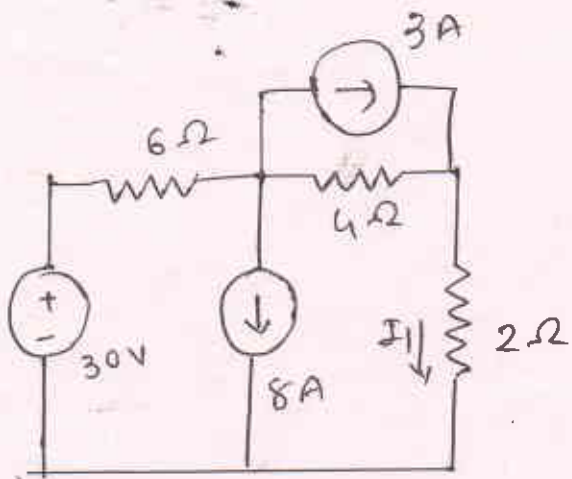


figure (9)

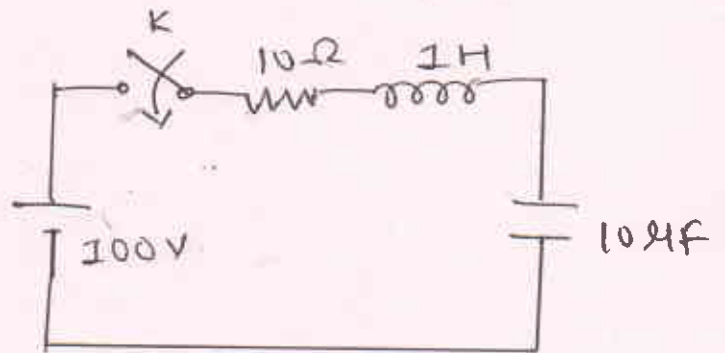


figure (10)

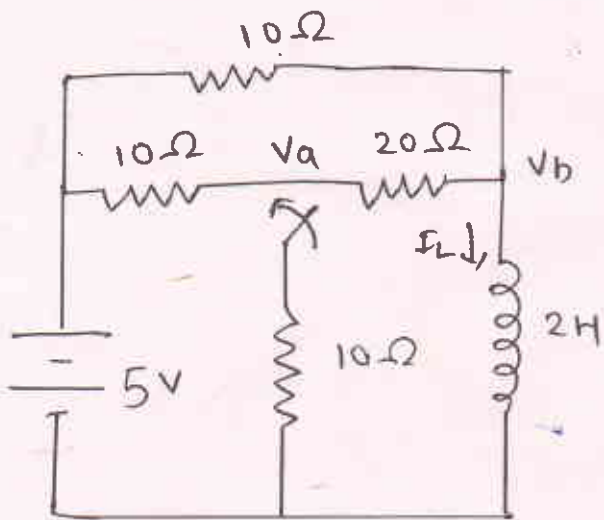


figure (11)