

QUESTION BANK

B.E. SEM IV EC

GUJARAT UNIVERSITY

Subject Name: EDC-II

Each Question is of 10 Marks.

- Que:1 Draw the circuit diagram of voltage shunt amplifier and derive an expression for input and output impedance.
- Que:2 What are the advantages of negative amplifiers? Explain them.
- Que:3 Draw the circuit diagram of voltage series amplifier and derive an expression for input and output impedance.
- Que:4 What are the advantages and disadvantages of positive amplifiers? Explain them.
- Que:5 Draw the circuit diagram of current shunt amplifier and derive an expression for input and output impedance.
- Que:6 Explain the concept of positive feedback. Also derive a term for gain with feedback.
- Que:7 Draw the circuit diagram of current series amplifier and derive an expression for input and output impedance.
- Que:8 Compare the advantages and disadvantages of negative and positive feedback amplifier.
- Que:9 Discuss the Barkhausen criterion as applied to electronic feedback oscillators. Why are LC oscillators not suitable for low frequency application?
- Que:10 Explain the working of Wein Bridge Oscillator with the help of circuit diagram. Derive the expression for frequency of oscillation. A wein bridge oscillator has a frequency of 500 kHz, if the value of C is 100pf, determine the value of R.
- Que:11 Derive the expression for the maximum efficiency of Class-B transformer coupled push pull amplifier.
- Que:12 Draw and explain complementary symmetry class B push pull amplifier.
- Que:13 Explain the working of Wein Bridge Oscillator with the help of circuit diagram. Derive the expression for frequency of oscillation. A wein bridge oscillator has a frequency of 500 kHz, if the value of C is 1000pF, determine the value of R.
- Que:14 What is power amplifier. Give the classification of power amplifier. Compare directly coupled class A and transformer coupled class A amplifier.
- Que:15 An amplifier has a midband gain A_{vmid} of 1000 with $f_L=50\text{Hz}$ and $f_H=50\text{Khz}$. If 5% feedback is applied then calculate
- 1) Gain with feedback
 - 2) f_L with feedback
 - 3) f_H with feedback
- Que:16 Derive the expression for maximum efficiency transformer couple class A amplifier.
- Que:17 Explain basic circuit principles for current controlled negative resistance device circuit, load line and equations.
- Que:18 What is tuned amplifier? Draw and explain double tuned amplifier.

- Que:19 With the help of V-I characteristics and load line, explain the monostable operation current controlled Negative resistance device.
- Que:20 Give the step by step procedure for identifying topology of feedback in an amplifier.
- Que:21 Design the RC elements of a Wien bridge oscillator for operation at $f_o = 10\text{kHz}$.
- Que:22 Which amplifiers are classified as power amplifier? Explain the general features of power amplifiers.
- Que:23 Draw the direct coupled class A amplifier and find the maximum efficiency.
- Que:24 Write short notes on:
- (i) LC Oscillator
 - (ii) RC phase shift Oscillator
 - (iii) Wein Bridge Oscillator
- Que:25 What is CMRR? Explain diode compensation technique for improving CMRR for emitter coupled differential amplifier.
- Que:26 A current series feedback amplifier circuit has an overall transconductance gain of -1mA/V , a voltage gain of -4 , and sensitivity of 50 . If $R_s = 1\text{K}\Omega$, $h_{fe} = 150$ and $r_{bb'}$ is negligible, find a) R_e b) R_L c) R_{if}
- Que:27 For a transistor colpitt oscillator, $L_3 = 100\mu\text{H}$, $C_1 = 0.005\mu\text{F}$ and $C_2 = 0.01\mu\text{F}$. Calculate the frequency of oscillation generated.
- Que:28 In Hartley oscillator calculate L_2 if $L_1 = 15\text{mH}$, $C = 50\text{pF}$, mutual inductance of coil is $5\mu\text{H}$ and frequency of oscillation is 168Hz .
- Que:29 Explain any two positive biased clamper circuit with necessary diagram and waveform.
- Que:30 Explain any two negative biased clamper circuit with necessary diagram and waveform.
- Que:31 Draw and explain transistor shunt voltage regulator with suitable diagram.
- Que:32 With the help of circuit diagram and waveform explain the application of a UJT as bistable circuit and monostable circuit.
- Que:33 Draw and explain shunt voltage regulator with necessary circuit and equation.
- Que:34 Explain double biased clipper with necessary circuits and waveforms.
- Que:35 Explain the emitter coupled clipper and draw its transfer characteristics.
- Que:36 With the help of circuit diagram explain the application of UJT as (i) Sawtooth generator (ii) stable circuit.
- Que:37 Write short notes on:
- (1) R-2R ladder type DAC
 - (2) Weighted resistor type DAC
- Que:38 Write short notes on:
- (1) Counter type A/D converter
 - (2) Flash-type A/D converter
- Que:39 Write short notes on:
- (1) Switched capacitor type DAC
 - (2) Successive approximation type ADC
- Que:40 Draw and explain block diagram of shunt regulator also explain zener and transistorized shunt regulator.